

# Preventing GaN Device VHF Oscillation

## APEC 2017

Zan Huang, Jason Cuadra

transphorm

Highest Performance, Highest Reliability GaN

# Parasitic oscillation


- Parasitic oscillation can occur in any switching circuit with fast-changing voltage and current that stimulate a parasitic LC network
- The oscillation becomes sustained when positive feedback with gain is present
  - The feedback could be through parasitic capacitance, parasitic inductance, shared or coupling inductance, etc.
  - Together with the device gain in the linear region, creates an oscillator
- Preventing oscillation in fast-switching GaN devices is more challenging than in silicon due to
  - Faster  $dv/dt$  and  $di/dt$
  - Higher transconductance
- Violent sustained VHF oscillation (50-200MHz) will cause destruction

# Sustained oscillation

- In a half-bridge circuit with high speed devices on both the high and low side, there are three steps that yield sustained oscillation on the high-side device during low-side device turn-on, and vice versa

Note: Sustained oscillation can occur even in a single-ended circuit, with very fast switching, e.g. a boost converter using a FET+diode; the analysis is similar to a half-bridge

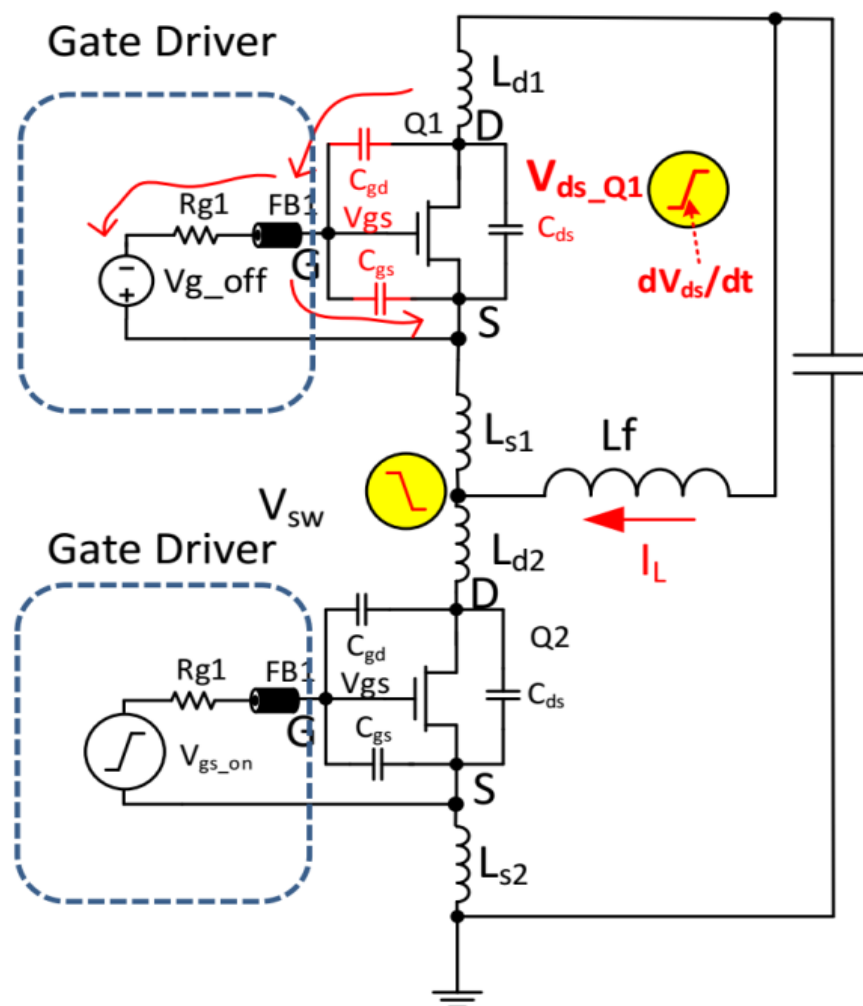
# Step 1: $V_{GS}$ change due to high $dv/dt$



- During low-side turn-on, the high-side FET is subjected to a large positive  $dv/dt$ , which couples through  $C_{GD}$  to increase  $V_{GS}$ , (“Miller effect”) reducing its off-voltage margin against gate threshold  $V_{TH}$
- To counter this, Transphorm devices are designed with a low ratio of  $C_{GD}$  to  $C_{GS}$  to minimize the Miller effect



 
## Step 2: $V_{GS}$ change due to high $di/dt$



- During low-side turn on, the high-side FET sees a decreasing current with a large negative  $di/dt$ , which multiplied by stray inductance  $L_s$  in the PCB layout, produces a voltage  $V_{Ls}$ , and also reduces the off-voltage margin
- It is necessary to have a tight layout and minimize the stray inductance
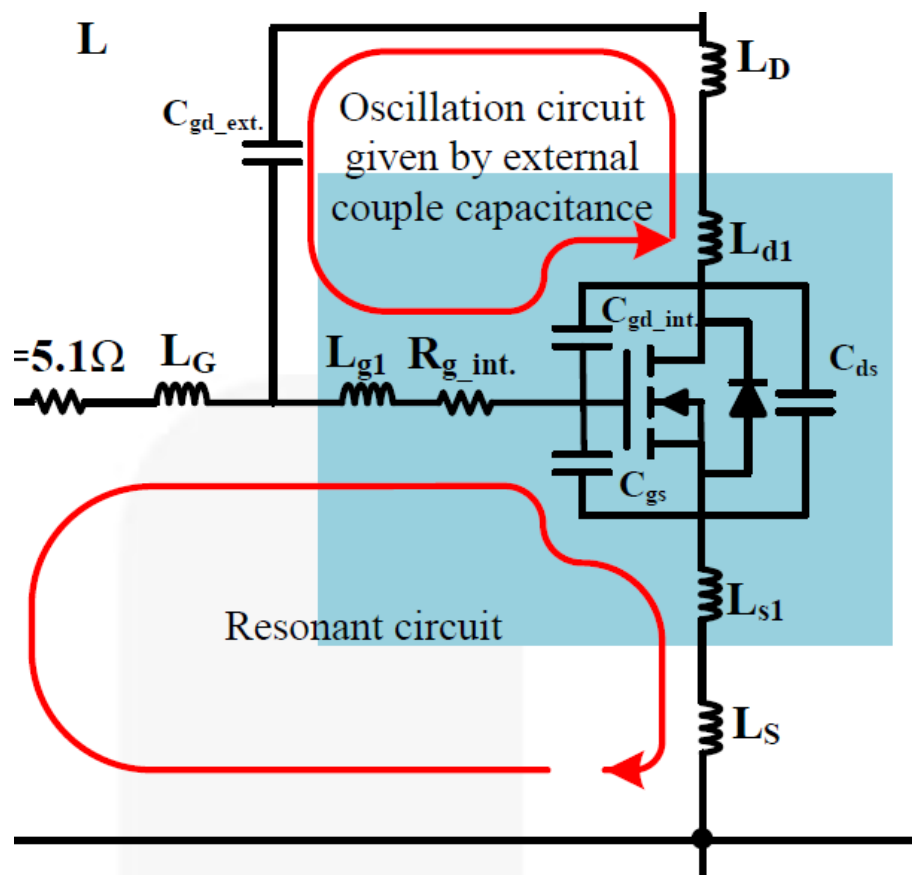
## Step 3: Amplification due to transconductance





- If  $V_{GS}$  is pulled above the threshold voltage  $V_{TH}$ , the device will operate in the linear region with transconductance  $g_m$ , which can be defined in below equation:

$$I_D = (V_{GS} - V_{TH}) * g_m$$

- The large gain in the feedback loop that includes external stray capacitance  $C_{gd\_ext}$  can then create a sustained oscillation

# The feedback loop transfer function

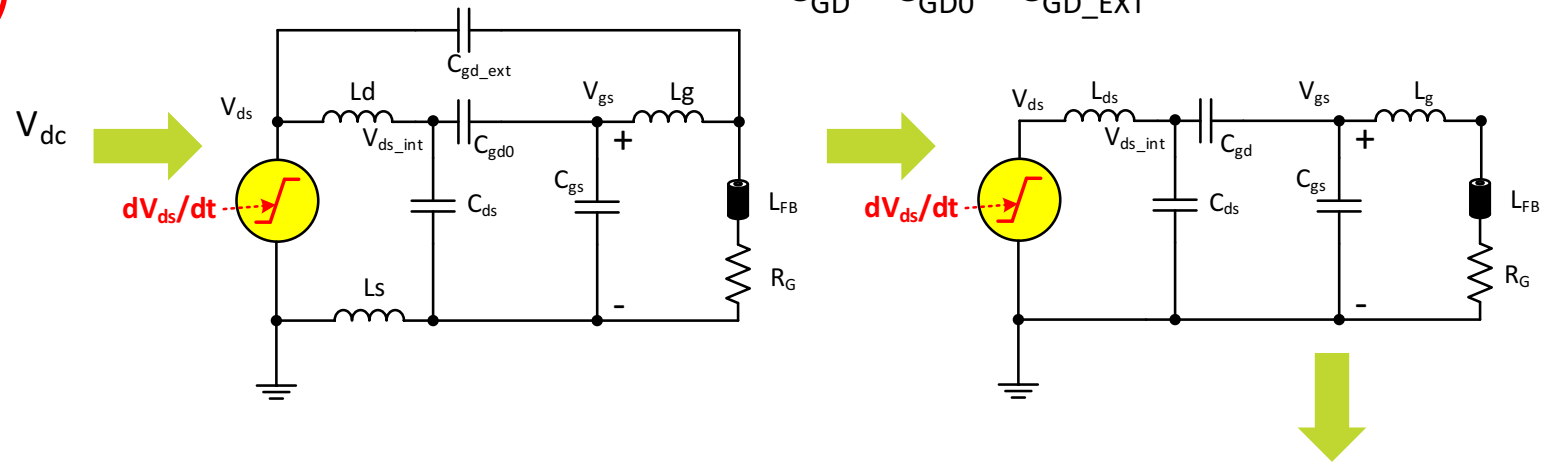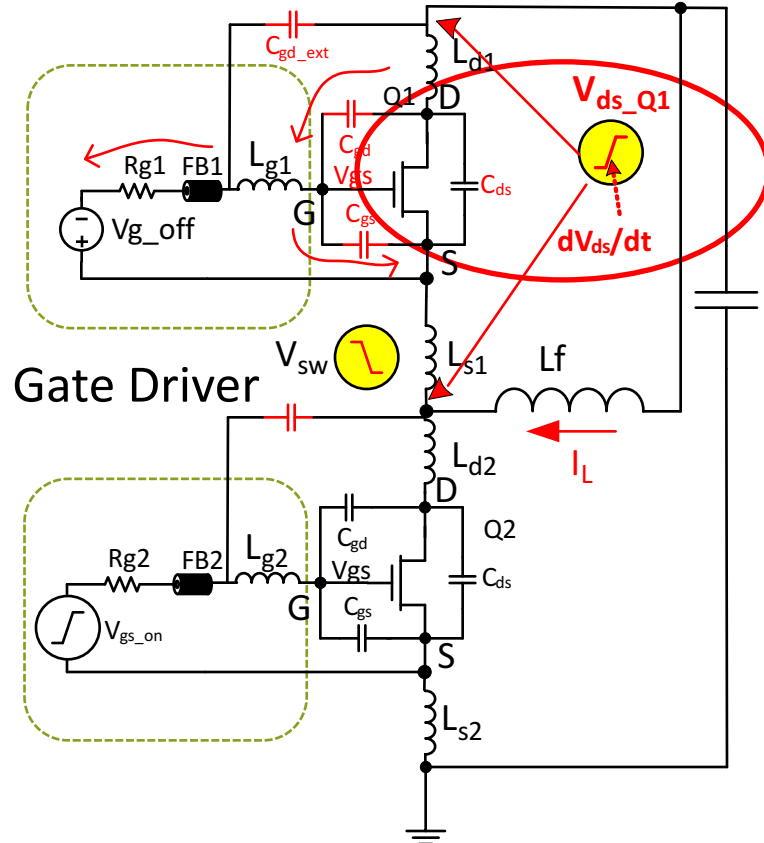


$$F(s) = \frac{V_{gs}(s)}{V_{ds}(s)} = sL_{ds} + \frac{s^2 L_{FB} C_{iss} + s R_g C_{iss} + 1}{s^3 L_{FB} (C_{iss} C_{DS} + C_{GS} C_{GD}) + s^2 R_g (C_{DS} C_{iss} + C_{GS} C_{GD}) + s C_{oss} + 1}$$


Where:  $C_{iss} = C_{GS} + C_{GD}$ ,  $C_{oss} = C_{DS} + C_{GD}$ , and  $L_{ds} = L_d + L_s$
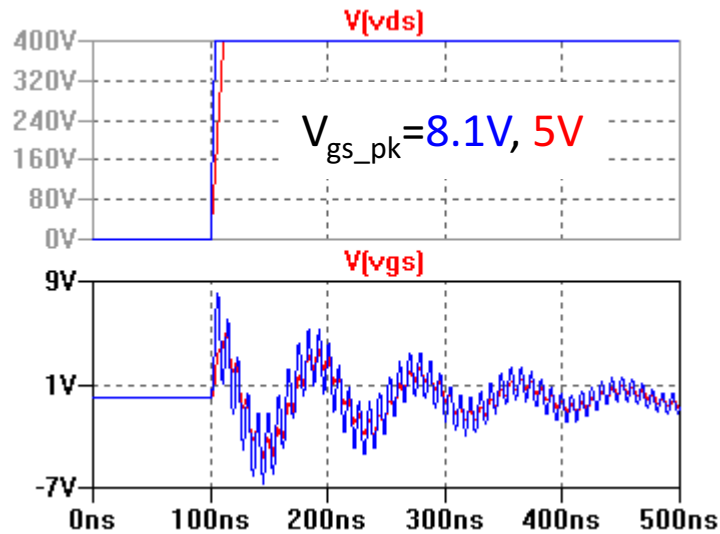
# Comparing ringing amplitude


$R_{G\_OFF}=1\Omega$ ,  $C_{GD\_EX}=2pF$   
Lead\_length=15mm (7.5nH)



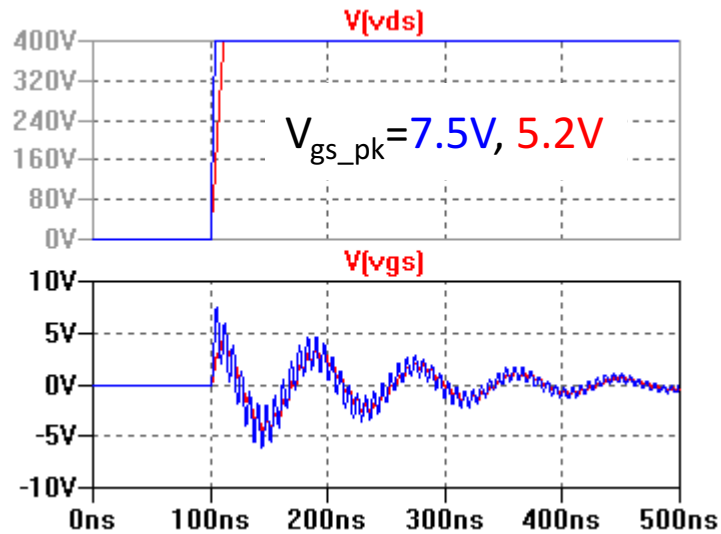$R_{G\_OFF}=1\Omega$ ,  $C_{GD\_EXT}=2pF$   
Lead\_length=10mm (5nH)



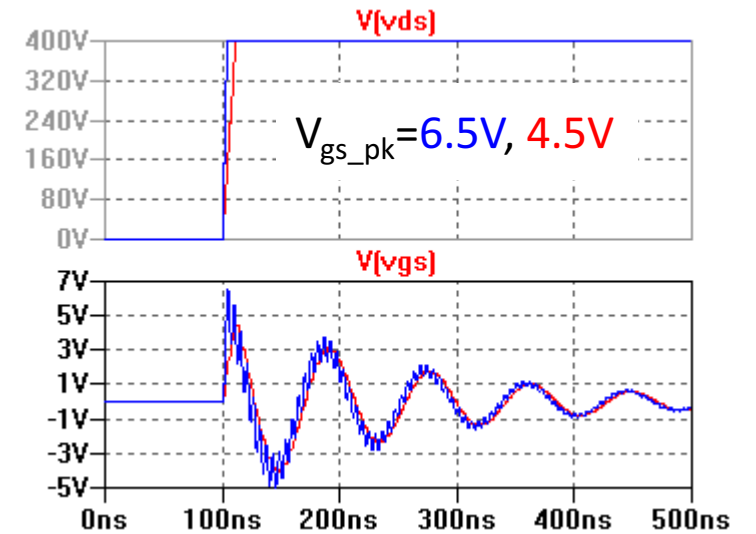$R_{G\_OFF}=1\Omega$ ,  $C_{GD\_EXT}=2pF$   
Lead\_length=5mm (2.5nH)



- Comparing blue and red curves, higher  $dV/dt$  increases the amplitude of the  $V_{GS}$  ringing
- Comparing different parasitic inductances, higher inductances increases the amplitude of the  $V_{GS}$  ringing

Red :  $dV_{DS}/dt=40V/ns$   
Blue :  $dV_{DS}/dt=100V/ns$



# To suppress the sustained oscillation


- Required
  - Optimize PCB layout
  - Use a ferrite bead in the gate
- Highly recommended
  - Add a ferrite bead to the drain
    - Improves efficiency because excessive ringing is lossy
- Optional
  - Add negative  $V_{g\_off}$  voltage
  - Reduce the turn-on  $dv/dt$
  - Add an RC snubber to damp the ringing energy
    - Slightly reduces efficiency

NOTE: The above can apply to a single-ended converter with very fast switching



## **Choosing a Drain Ferrite Bead**

## Example: Bridge circuit

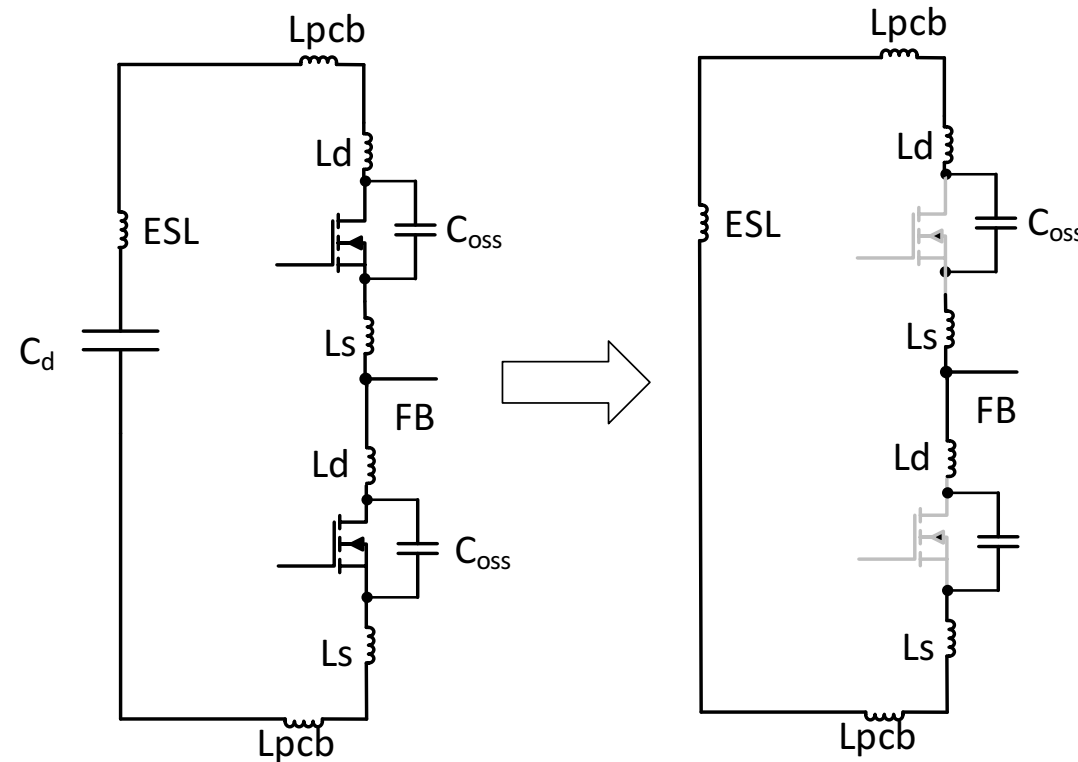


- The equivalent LC resonant loop that largely determines the power loop oscillation frequency


$$L = 2 * L_D + 2 * L_S + ESL + L_{PCB} + L_{WIRE}$$

$C = C_{OSS}$ , (one  $C_{OSS}$  is bypassed when device is conducting)
 
# Adding the ferrite bead into the circuit




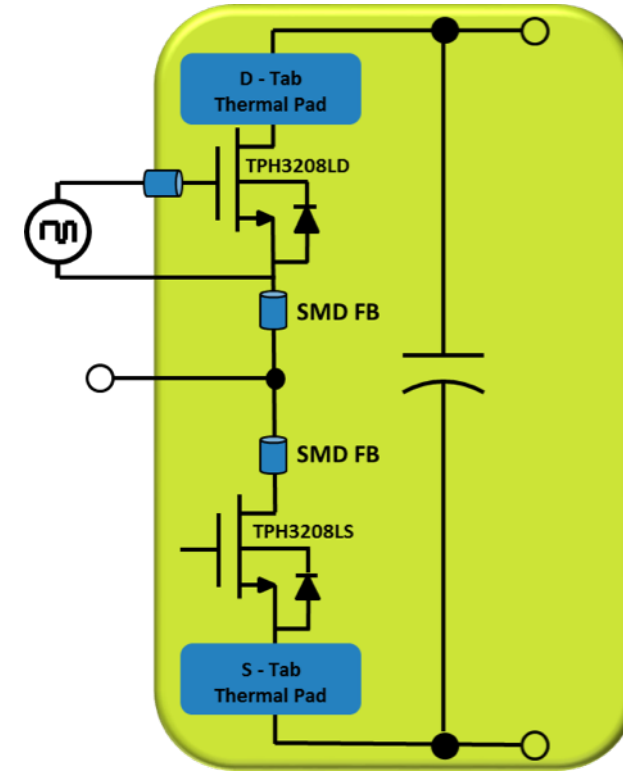‘Ring’ (through-hole) type of the ferrite bead can be placed on through-hole type device’s D pin




SMD type of ferrite bead should be placed on PCB without interfering with the heat dissipation from the large pad (drain for TPHxxxLD part, source for TPHxxxLS part)


# Transphorm PQFN Package Variations

 
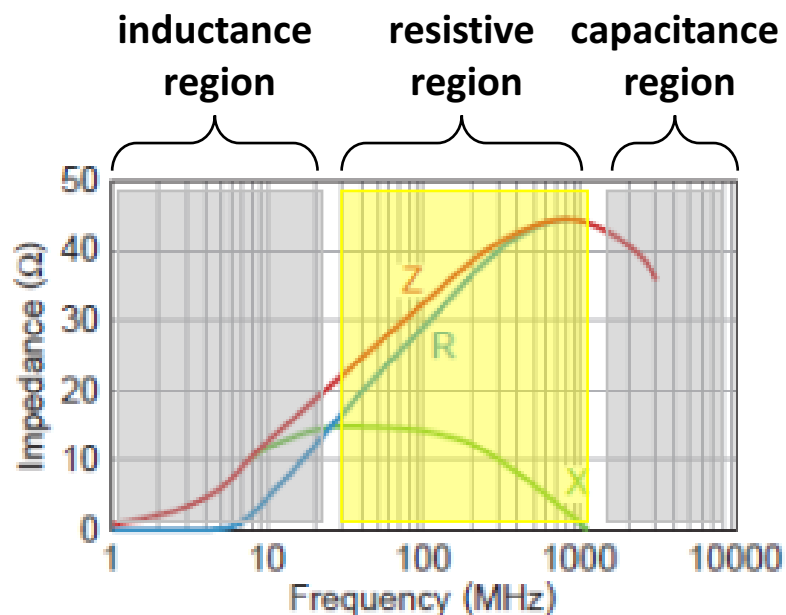
# Choose a ferrite bead as a damping resistor at the ringing frequency (50-200MHz)



 Choose the ferrite bead that **R>X** @50-200MHz, so the ferrite bead shows more resistive than inductive in this region



For a series LCR circuit, the damping factor is given by:

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

For critical damping, R should be:

$$R = 2\zeta \sqrt{\frac{L}{C}} = 2 * 1 * \sqrt{\frac{25nH}{110pF}} = 30\Omega$$


So use a bead with >30Ω@100MHz for each device



# Verifying the result

Note the  
ringing

NO DRAIN BEAD

 


Choke current

Half-bridge output  
voltage (low-side  $V_{DS}$ )

ZOOM of above

Note the  
ringing is well  
damped

WITH DRAIN BEAD

 


Choke current

Half-bridge output  
voltage (low-side  $V_{DS}$ )

ZOOM of above
 
# TPH3212 HB low side switching w/o FB


TPH3212PS B5L005-1 78976-01 150602AC-6 Dev#0 400V Lowside Switching with No Snubber




Turn off at 16A,  
voltage spike damped  
to <20% after 3 cycles:  
**Stable**

Turn off at 18A,  
voltage spike damped  
to >20% after 3 cycles:  
**Almost unstable**

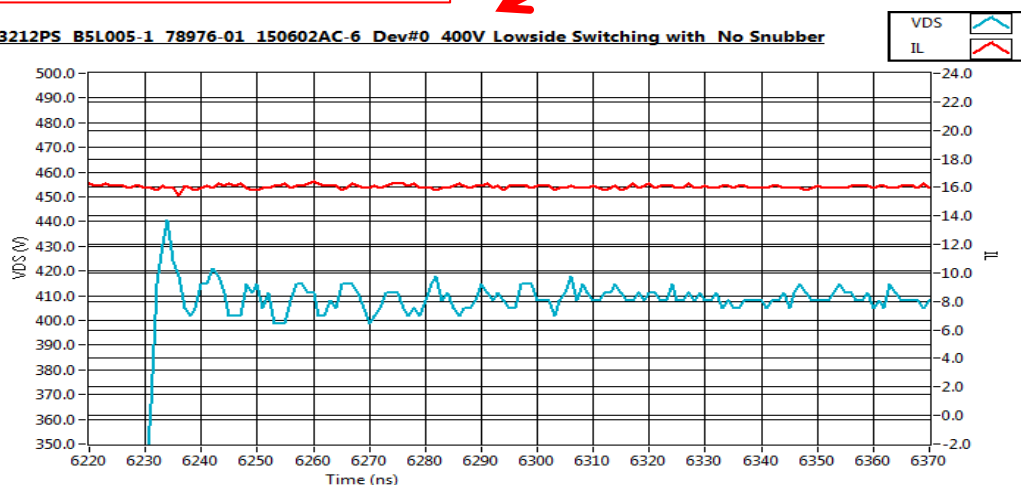TPH3212PS B5L005-1 78976-01 150602AC-6 Dev#0 400V Lowside Switching with No Snubber




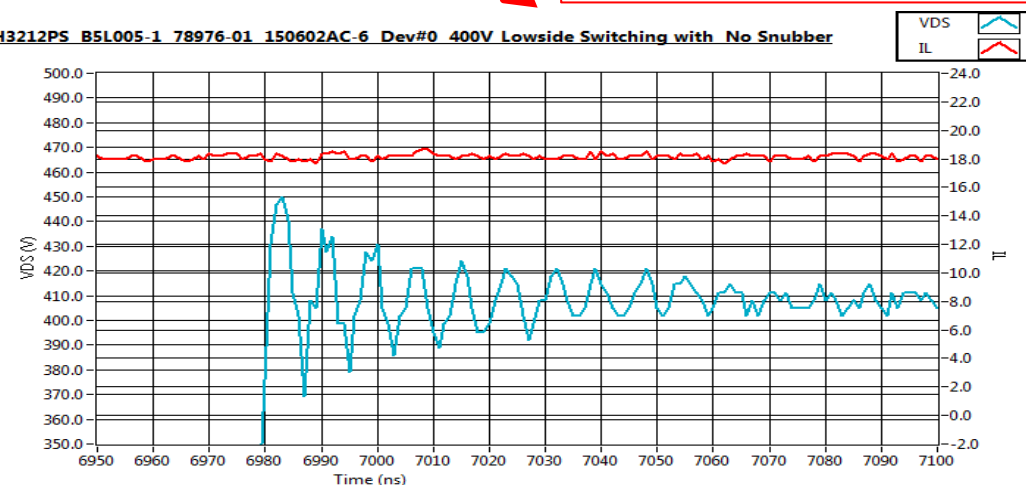TPH3212PS B5L005-1 78976-01 150602AC-6 Dev#0 400V Lowside Switching with No Snubber



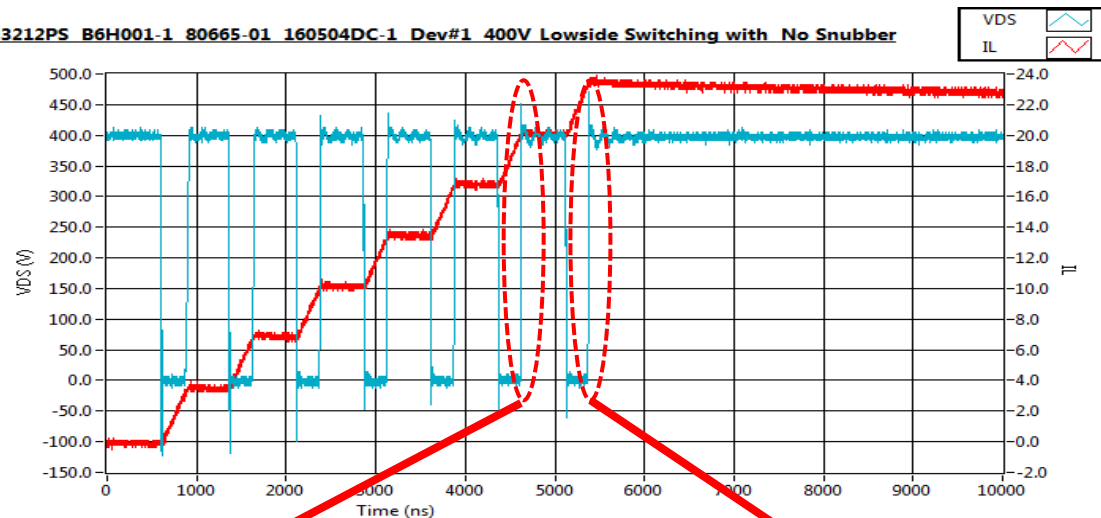
# TPH3212 HB low side switching w/ FB


TPH3212PS B6H001-1 80665-01 160504DC-1 Dev#1 400V Lowside Switching with No Snubber



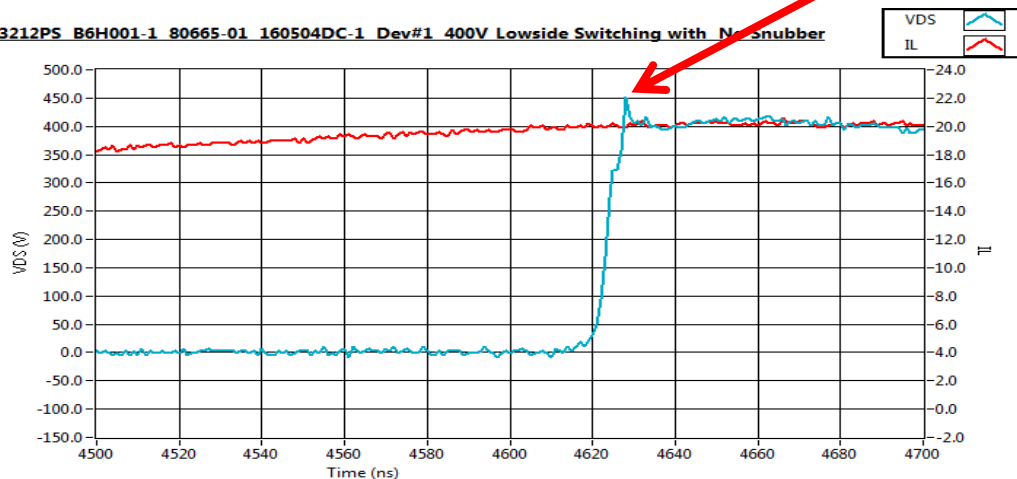TPH3212PS B6H001-1 80665-01 160504DC-1 Dev#1 400V Lowside Switching with No Snubber



 TPH3212PS B6H001-1 80665-01 160504DC-1 Dev#1 400V Lowside Switching with No Snubber



Turn off at 20 and 24A, no ringing: **Stable**

## $V_{TDS}$ rating

- Using a drain ferrite bead does increase the drain spike voltage
- However, all Transphorm devices are specified with  $V_{TDS}$  (transient  $V_{DS}$ ) which is 150V higher than the rated max DC  $V_{DS}$
- Transphorm devices are guaranteed to operate safely under repetitive spike voltages within the datasheet specification, making it more suitable for the drain ferrite bead solution

# TPH3212PS

## Absolute Maximum Ratings ( $T_C=25^\circ\text{C}$ unless otherwise stated)

Symbol	Parameter		Limit Value	Unit
$I_{D25^\circ\text{C}}$	Continuous drain current @ $T_C=25^\circ\text{C}$ <sup>a</sup>		26.5	A
$I_{D100^\circ\text{C}}$	Continuous drain current @ $T_C=100^\circ\text{C}$ <sup>a</sup>		16.5	A
$I_{DM}$	Pulsed drain current (pulse width: 10 $\mu\text{s}$ )		120	A
$V_{DSS}$	Drain to source voltage		650	V
$V_{TDS}$	Transient drain to source voltage <sup>b</sup>		800	V
$V_{GSS}$	Gate to source voltage		$\pm 18$	V
$P_{D25^\circ\text{C}}$	Maximum power dissipation		104	W
$T_C$	Operating temperature	Case	-55 to +150	$^\circ\text{C}$
$T_J$		Junction	-55 to +150	$^\circ\text{C}$
$T_S$	Storage temperature		-55 to +150	$^\circ\text{C}$
$T_{CSOLD}$	Soldering peak temperature <sup>c</sup>		260	$^\circ\text{C}$

## Thermal Resistance

Symbol	Parameter	Typical	Unit
$R_{\theta JC}$	Junction-to-case	1.2	$^\circ\text{C/W}$
$R_{\theta JA}$	Junction-to-ambient	62	$^\circ\text{C/W}$


Notes:

- For high current operation, see application note AN0009
- In off-state, spike duty cycle  $D < 0.01$ , spike duration  $< 1\mu\text{s}$
- For 10 sec., 1.6mm from the case







# Layout with TO247 Packages

 

  
# Switching 400V/100A with Clean Waveform



# 200V:400V Boost Converter


## 5.5kW and 98.8% Peak Efficiency

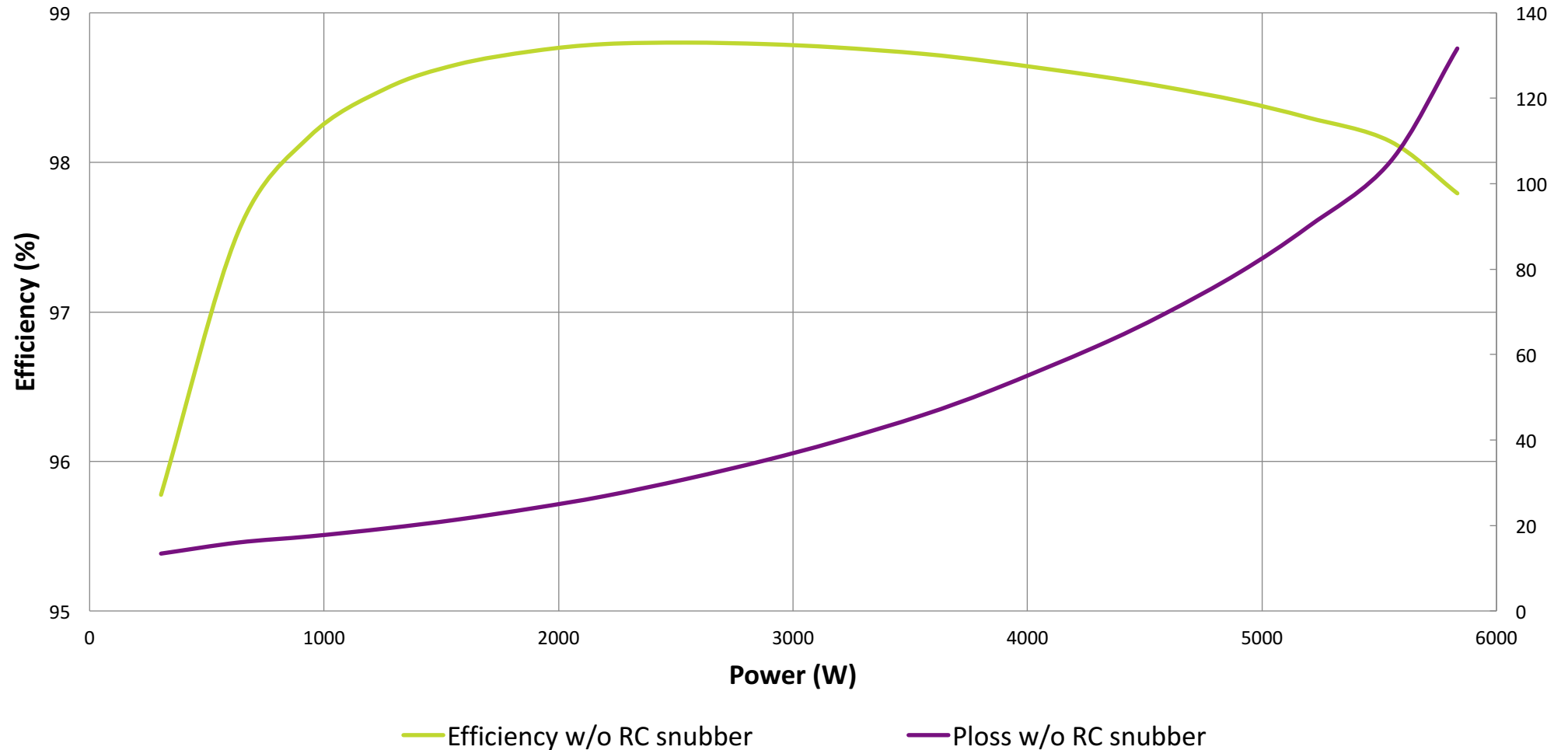
 
# Silicon Valley Center of Excellence

**Design Tools:** Evaluation kits, reference designs, simulation models (SPICE)

**Support:** Global field applications team, Q+R testing, system component selection analysis, technical marketing



**Education:** EMI control methods, high power app concepts, optimization techniques, topology comparisons, etc.

**Technical Library:** Application notes, design guides, PCB layouts, schematics, technical white papers



Thank You!

transphorm

Highest Performance, Highest Reliability GaN